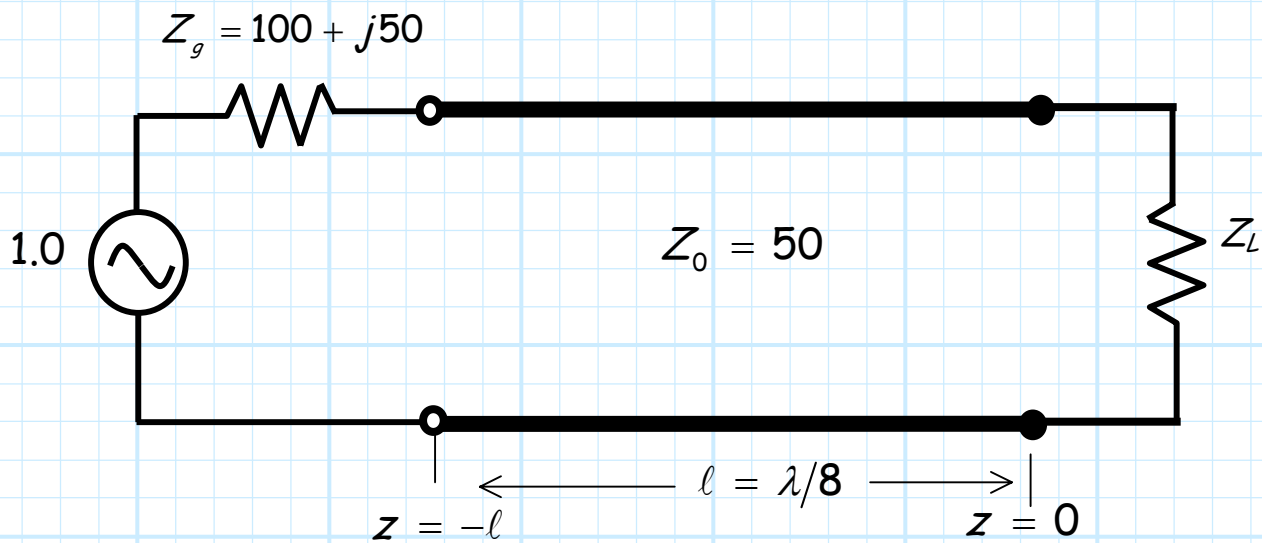


Special Problem 2.6-2

Determine the value of load Z_L that will result in the maximum absorbed power.

How much power would this be?



Hint: a Smith Chart comes in handy!