

Special Problem 2.6-6

For this particular circuit, the power **absorbed** by load R_L can be **maximized** by simply selecting the correct value of the **purely reactive** element (jX).

Determine this reactance value X .

Hint: the answer is **not** $X = -10$!

