

Special Problem 4.2 -1

Determine the **impedance matrix** of this three-port device:

