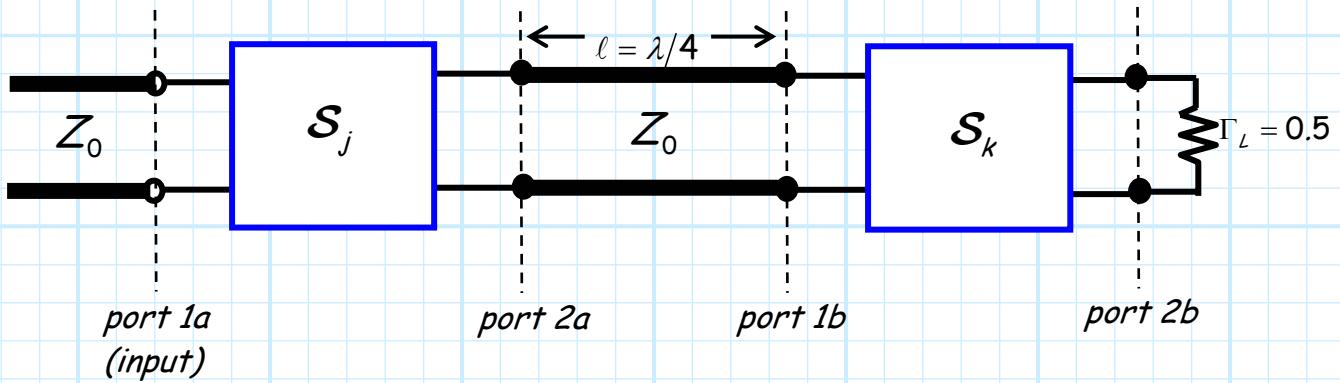


Special Problem 4.5-4

Below is a single-port device (with input at port 1a) constructed with two two-port devices (\mathcal{S}_j and \mathcal{S}_k), a quarter wavelength transmission line, and a load impedance.



The scattering matrices of the two-port devices are:

$$\mathcal{S}_j = \begin{bmatrix} 0.35 & 0.5 \\ 0.5 & 0 \end{bmatrix} \quad \mathcal{S}_k = \begin{bmatrix} 0 & 0.8 \\ 0.8 & 0.4 \end{bmatrix}$$

Using the nodes below, draw the complete signal flow graph of this circuit.

Then reduce the graph (on the next page!) to determine the return loss at the input port.

