

### Special Problem 7.2-2

For the three-port network below, determine the value of resistor  $R_1$  required to make  $S_{11} = 0$ .

