

Special Problem 7.3-3

Perform an **even-odd** mode analysis on the circuit below to find the value of voltage v_3 .

You must use even-odd mode analysis to find the answer!

Hint: Recall that one 100 ohm resistor is equivalent to two 50 ohm resistors in series.

