

Special Problem 7.3-5

Carefully (**very** carefully) consider the **symmetric** 4-port network below.

The two **transmission lines** have a characteristic impedance of $Z_0 = 50\ \Omega$. The bottom conductor for each transmission line is connected to ground and is not shown.

Use **odd-even mode analysis** to determine the value of admittance parameter Y_{11} .

