

## Special Problem 8.5-1

You have designed a **low-pass filter** with **lumped elements**, and now wish to approximate the design with **distributed elements**.

But instead of using Richard's Transformation, you decide to use **Stiles' Transformation!**

The Stiles transformation is **similar** to the Richard's transformation, in that it uses **shorted** and **open stubs** to approximate capacitors and inductors.

However, in the Stiles transformation, the **electrical length** of each stub **must be**  $\beta_c l = 2\pi/3$  ( $\beta_c l = 120^\circ$ ), where  $\beta_c = \omega_c/v_p$ , and  $\omega_c$  is the cutoff frequency of the low-pass filter.

Determine the distributed element **design** for the Stiles transformation to replace:

a) an inductor  $L$

b) a capacitor  $C$

Specifically, determine the **type of stub** required for each design (open or short) and the **characteristic impedance** of each stub in terms of the lumped element value ( $L$  or  $C$ ), and cutoff frequency  $\omega_c$ .

Remember, the electrical length of each stub **must be**  $\beta_c l = 2\pi/3$  ( $\beta_c l = 120^\circ$ )!