

## 5.4 - The Quarter-Wave Transformer

**Reading Assignment: pp. 73-76, 240-243**

By now you've noticed that a **quarter-wave length** of transmission line ( $l = \lambda/4$ ,  $2\beta l = \pi$ ) appears **often** in microwave engineering problems.

Another application of the  $l = \lambda/4$  transmission line is as an **impedance matching network**.

**HO: THE QUARTER-WAVE TRANSFORMER**


**HO: THE SIGNAL-FLOW GRAPH OF A QUARTER-WAVE TRANSFORMER**

**Q:** *Why does the quarter-wave matching network work—after all, the quarter-wave line is **mismatched** at both ends?*

**A:** **HO: MULTIPLE REFLECTION VIEWPOINT**

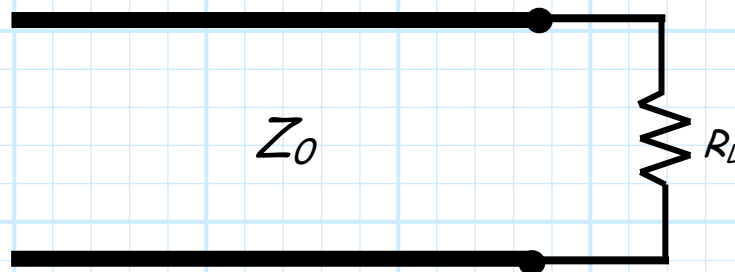
# The Quarter-Wave Transformer

Say the end of a transmission line with characteristic impedance  $Z_0$  is terminated with a **resistive** (i.e., real) load.




Unless  $R_L = Z_0$ , the resistor is **mismatched** to the line, and thus some of the incident power will be **reflected**.

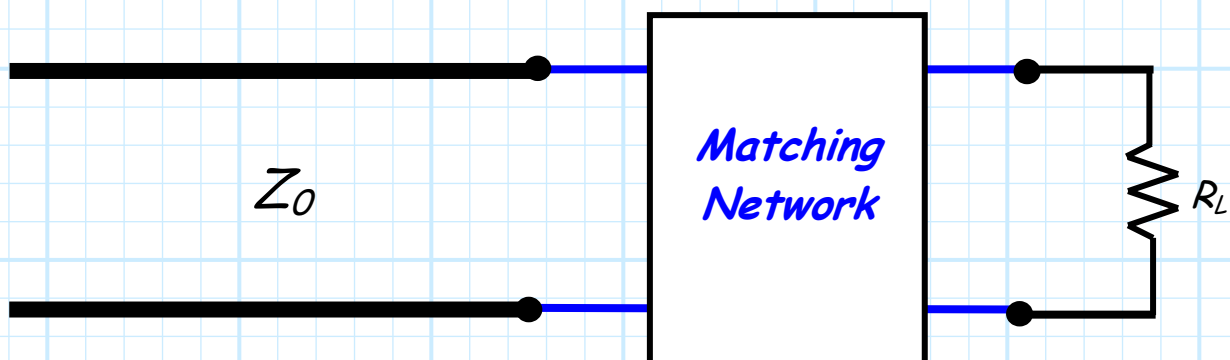We can of course correct this situation by placing a matching network between the line and the load:



In addition to the designs we have just studied (e.g., L-networks, stub tuners), one of the simplest matching network designs is the **quarter-wave transformer**.

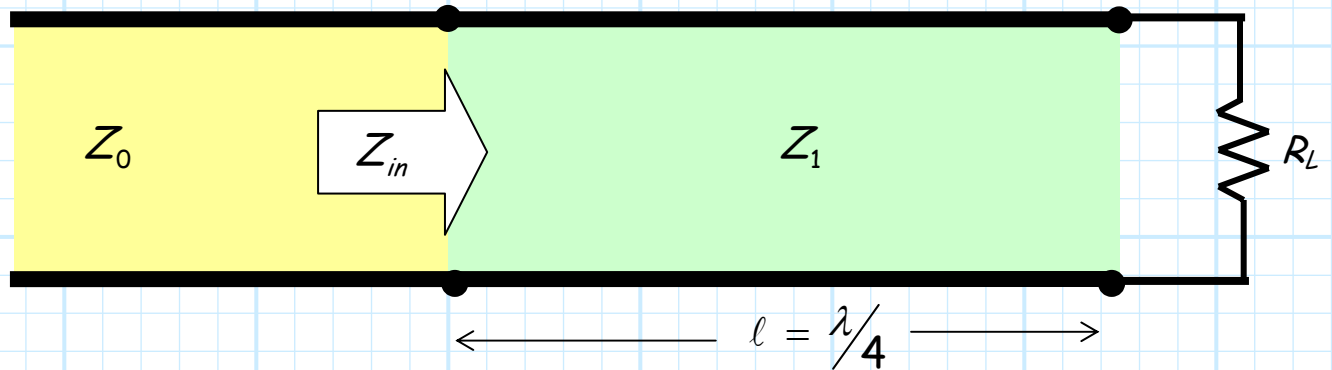The quarter-wave transformer is simply a transmission line with characteristic impedance  $Z_1$  and length  $\ell = \lambda/4$  (i.e., a quarter-wave line).



The  $\lambda/4$  line is the **matching network!**

**Q:** *But what about the characteristic impedance  $Z_1$ ; what should its value be??*

**A:** Remember, the quarter wavelength case is one of the **special** cases that we studied. We know that the **input** impedance of the quarter wavelength line is:

$$Z_{in} = \frac{(Z_1)^2}{Z_L} = \frac{(Z_1)^2}{R_L}$$

Thus, if we wish for  $Z_{in}$  to be numerically equal to  $Z_0$ , we find:

$$Z_{in} = \frac{(Z_1)^2}{R_L} = Z_0$$

Solving for  $Z_1$ , we find its **required** value to be:


$$(Z_1)^2 / R_L = Z_0$$

$$(Z_1)^2 = Z_0 R_L$$

$$Z_1 = \sqrt{Z_0 R_L}$$

In other words, the characteristic impedance of the quarter wave line is the **geometric average** of  $Z_0$  and  $R_L$ !

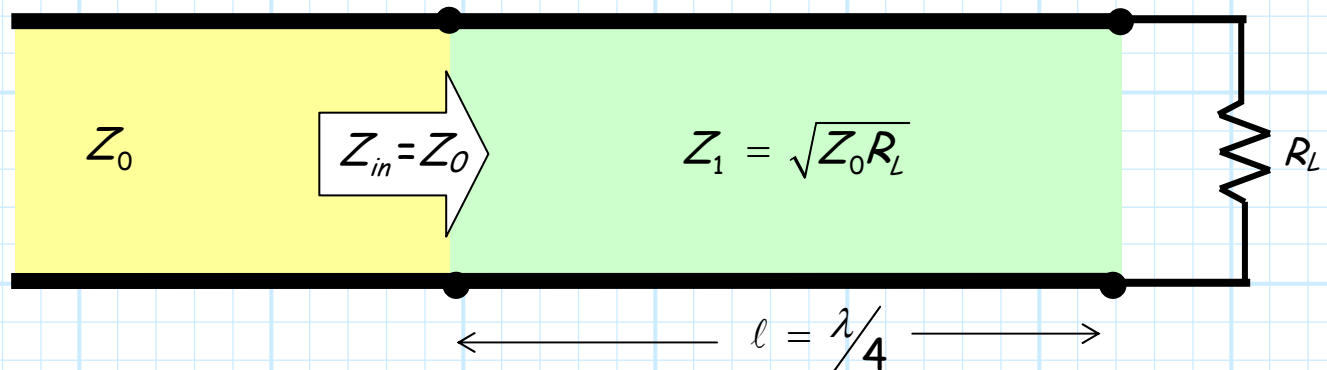Therefore, a  $\lambda/4$  line with characteristic impedance  $Z_1 = \sqrt{Z_0 R_L}$  will **match** a transmission line with characteristic impedance  $Z_0$  to a resistive load  $R_L$ .



Thus, **all power** is delivered to load  $R_L$ !

Alas, the quarter-wave transformer (like all our designs) has a few problems!

## Problem #1

The matching **bandwidth** is **narrow** !

In other words, we obtain a **perfect** match at precisely the frequency where the length of the matching transmission line is a **quarter-wavelength**.

→ But remember, this length can be a quarter-wavelength at just **one** frequency!

Remember, **wavelength** is related to **frequency** as:

$$\lambda = \frac{v_p}{f} = \frac{1}{f\sqrt{LC}}$$


where  $v_p$  is the **propagation velocity** of the wave .

For **example**, assuming that  $v_p = c$  ( $c$  = the speed of light in a vacuum), one wavelength at 1 GHz is 30 cm ( $\lambda = 0.3$  m), while one wavelength at 3 GHz is 10 cm ( $\lambda = 0.1$  m). As a result, a transmission line length  $\ell = 7.5$  cm is a quarter wavelength for a signal at 1GHz **only**.

Thus, a quarter-wave transformer provides a **perfect** match ( $\Gamma_{in} = 0$ ) at **one and only one** signal frequency!

As the signal frequency (i.e., wavelength) changes, the **electrical** length of the matching transmission line changes. It will **no longer** be a **quarter** wavelength, and thus we **no longer** will have a **perfect** match.

We find that the **closer**  $R_L$  ( $R_{in}$ ) is to characteristic impedance  $Z_0$ , the **wider** the bandwidth of the quarter wavelength transformer.

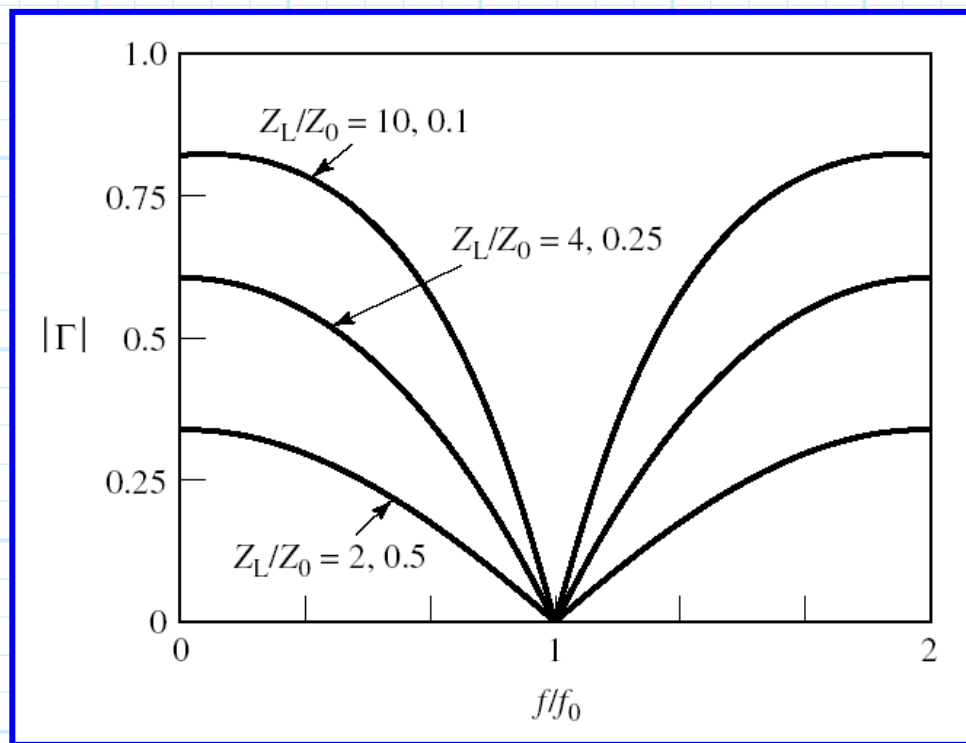

**Figure 5.12 (p. 243)** Reflection coefficient magnitude versus frequency for a single-section quarter-wave matching transformer with various load mismatches.

We will find that the bandwidth can be **increased** by adding **multiple**  $\lambda/4$  sections!


## Problem #2

Recall the matching solution was limited to loads that were **purely real!** I.E.:

$$Z_L = R_L + j0$$


Of course, this is a **BIG** problem, as most loads will have a **reactive** component!

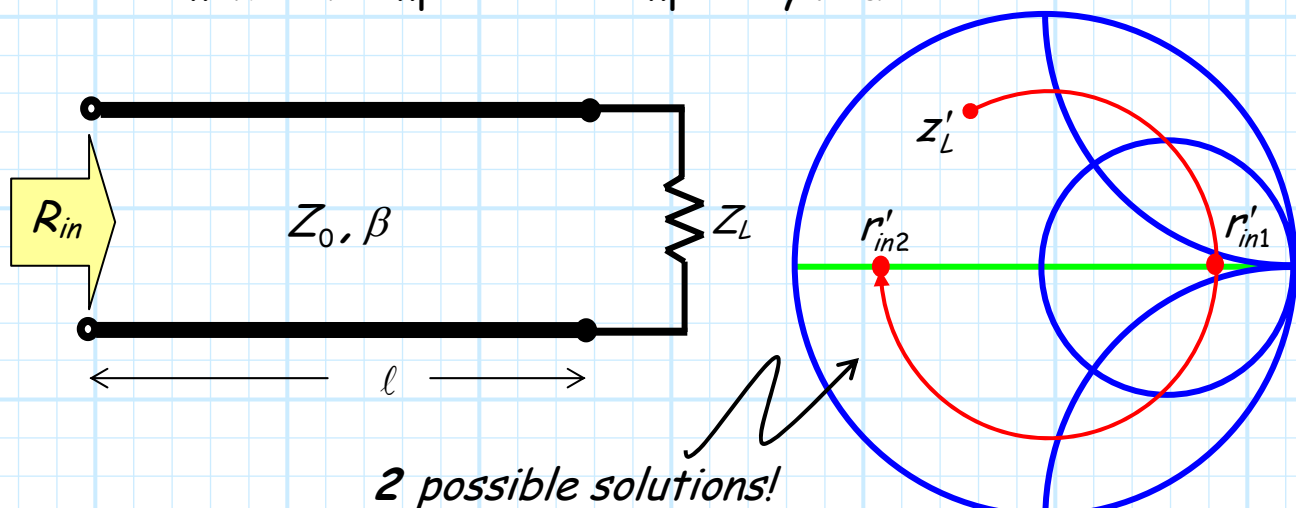Fortunately, we have a relatively easy **solution** to this problem, as we can always add some **length**  $\ell$  of transmission line to the load to make the impedance completely **real**:



However, remember that the input impedance will be purely real at only **one** frequency!

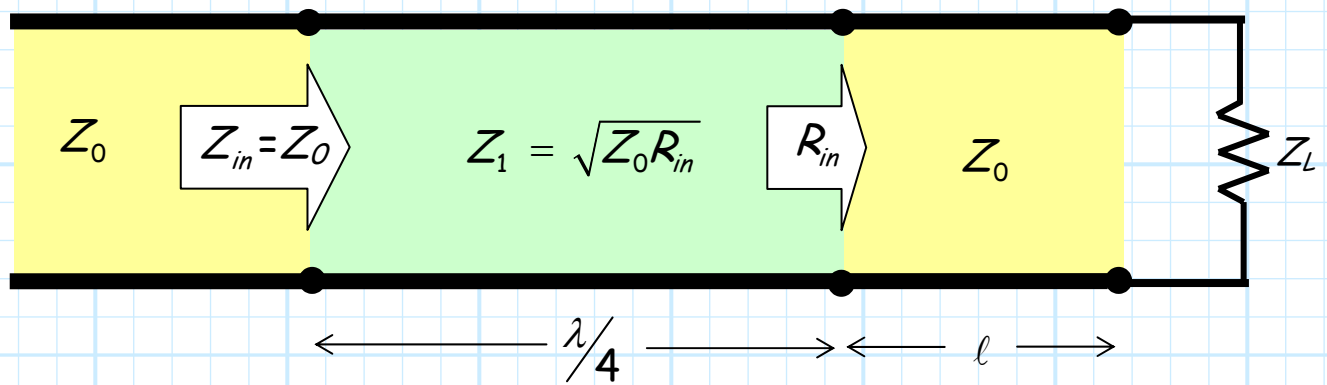We can then build a quarter-wave transformer to **match** the line  $Z_0$  to resistance  $R_{in}$ :




Again, since the transmission lines are lossless, **all** of the incident power is delivered to the **load**  $Z_L$ .



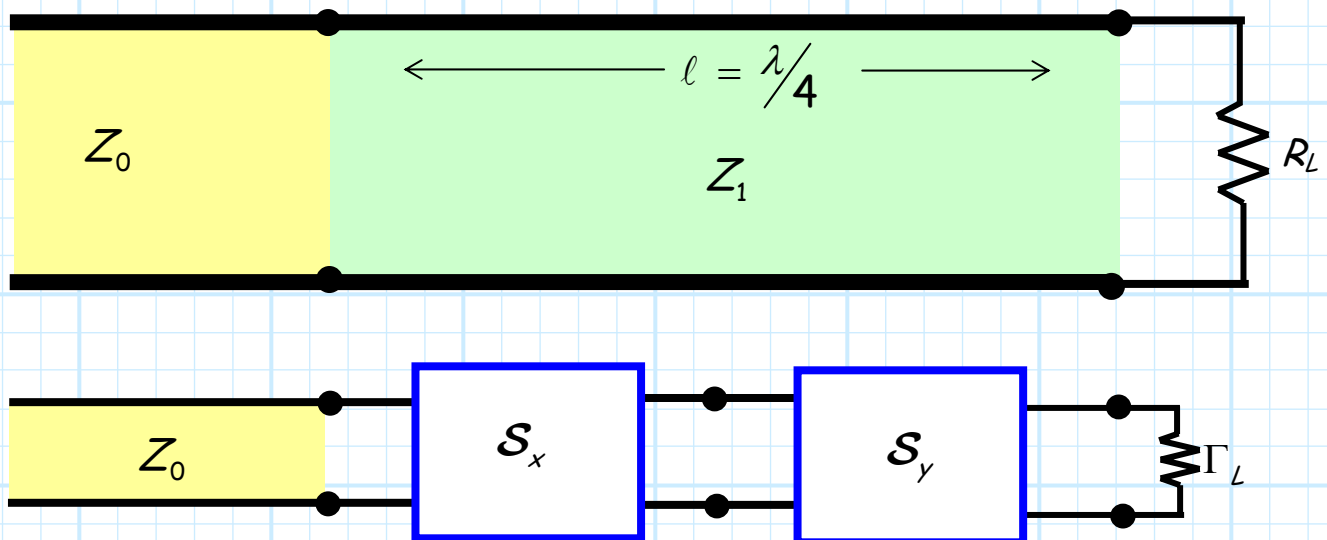
# The Signal Flow Graph of a Quarter-Wave Transformer

A quarter wave transformer can be thought of as a cascaded series of two two-port devices, terminated with a load  $R_L$ :



**Q:** *Two two-port devices? It appears to me that a quarter-wave transformer is **not** that complex. What **are** the two two-port devices?*

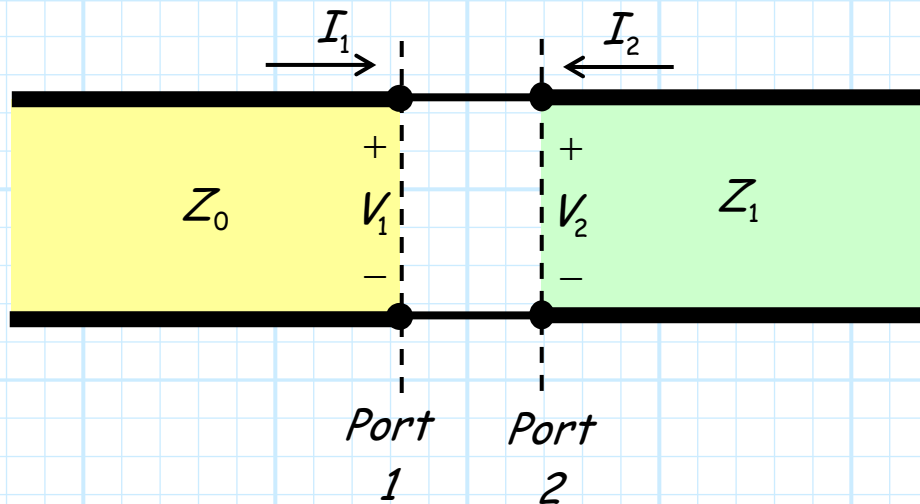**A:** The first is a "connector". Note a connector is the interface between one transmission line (characteristic impedance  $Z_0$ ) to a second transmission line (characteristic impedance  $Z_1$ ).



Recall that we **earlier** determined the scattering matrix of this two-port device:


$$S_x = \begin{bmatrix} \frac{Z_1 - Z_0}{Z_1 + Z_0} & \frac{2\sqrt{Z_0 Z_1}}{Z_0 + Z_1} \\ \frac{2\sqrt{Z_0 Z_1}}{Z_0 + Z_1} & \frac{Z_0 - Z_1}{Z_0 + Z_1} \end{bmatrix}$$

This result can be more **compactly** stated as:


$$S = \begin{bmatrix} \Gamma & T \\ T & -\Gamma \end{bmatrix}$$

where  $\Gamma \doteq \frac{Z_1 - Z_0}{Z_1 + Z_0}$  and  $T \doteq \frac{2\sqrt{Z_0 Z_1}}{Z_0 + Z_1}$

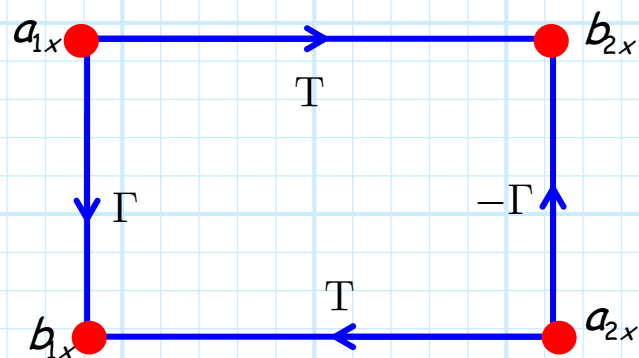The signal flow graph of this device is therefore:




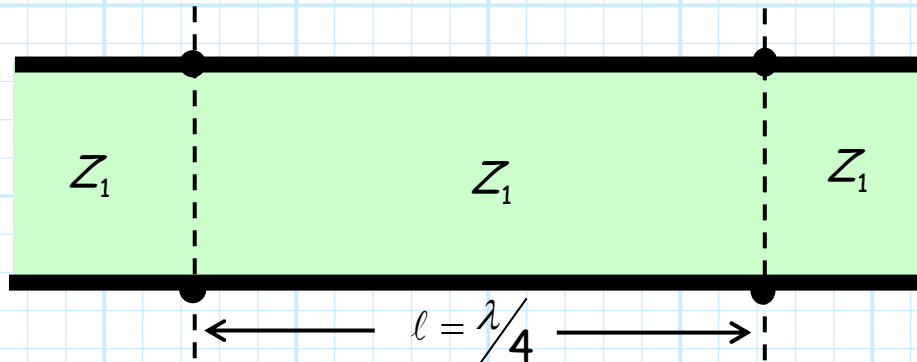Now, the second two-port device is a quarter wavelength of transmission line.




We know that it has the scattering matrix:

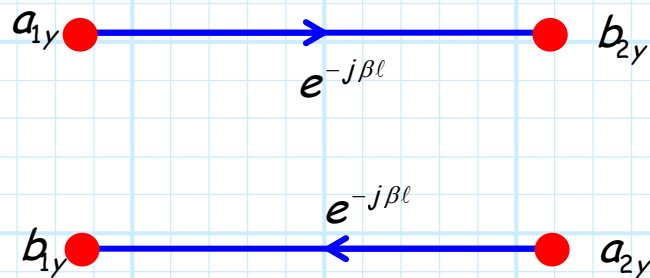
$$S_y = \begin{bmatrix} 0 & e^{-j\beta l} \\ e^{-j\beta l} & 0 \end{bmatrix}$$



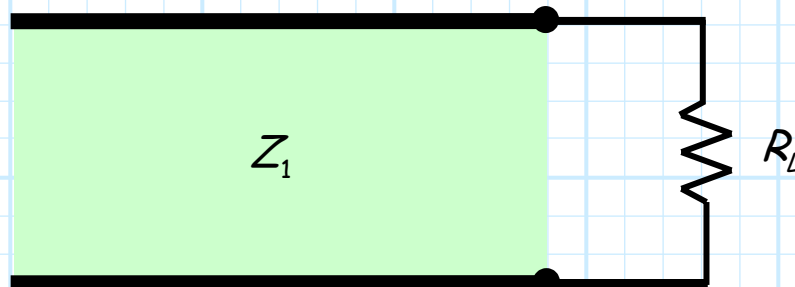
Finally, a load has a "scattering matrix" of:


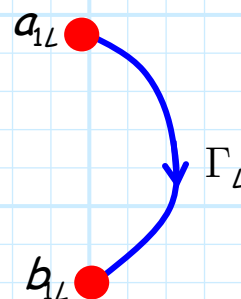
$$S = \left[ \frac{R_L - Z_1}{R_L + Z_1} \right] = \Gamma_L$$



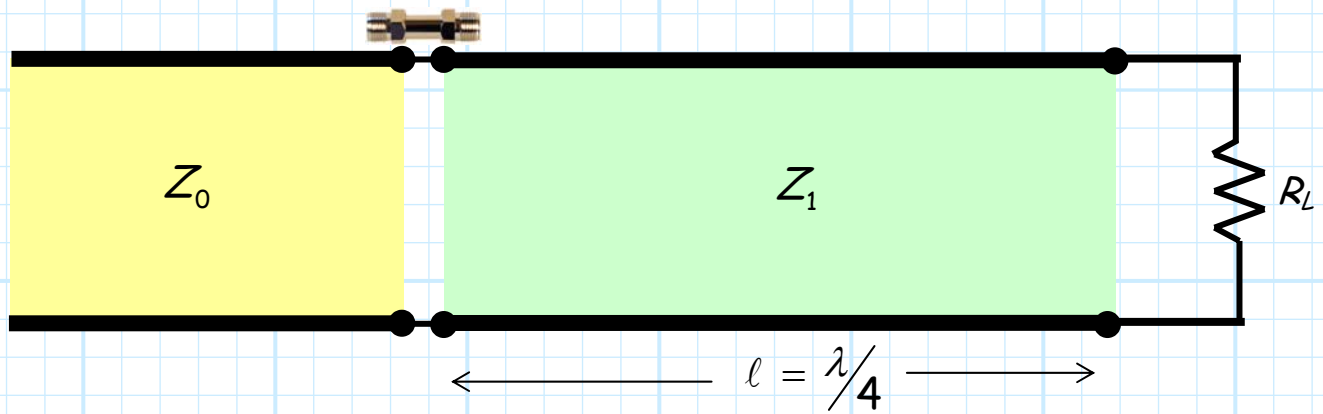
Of course, if we connect the ideal connector to a quarter wavelength of transmission line, and terminate the whole thing with load  $R_L$ , we have formed a **quarter wave matching network!**




The boundary conditions associated with these connections are likewise:

$$a_{1y} = b_{2x} \quad a_{2x} = b_{1y} \quad a_{1L} = b_{2y} \quad a_{2y} = b_{1L}$$

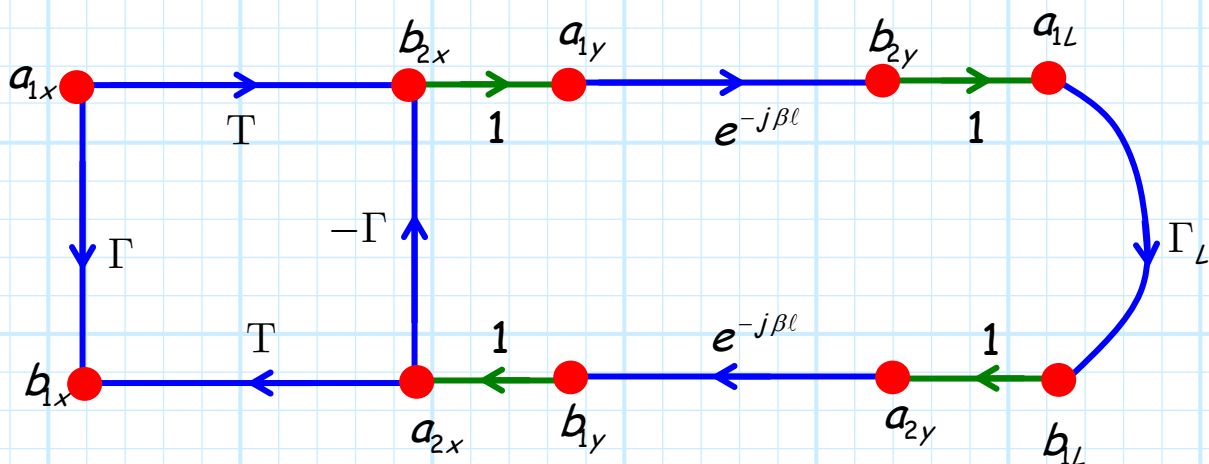We can thus put the signal-flow graph pieces together to form the **signal-flow graph** of the quarter wave network:




And simplifying:

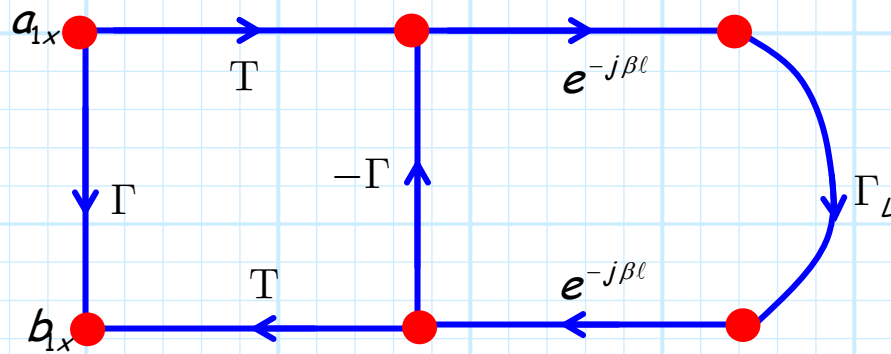


Now, let's see if we can **reduce** this graph to determine:

$$\Gamma_{in} \doteq \frac{b_{1x}}{a_{1x}}$$


From the **series** rule:

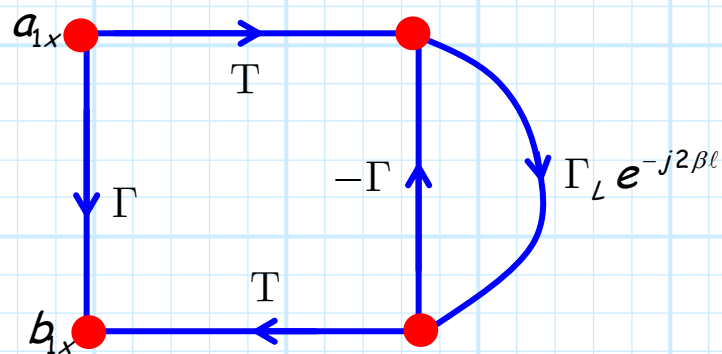


From the **splitting** rule:

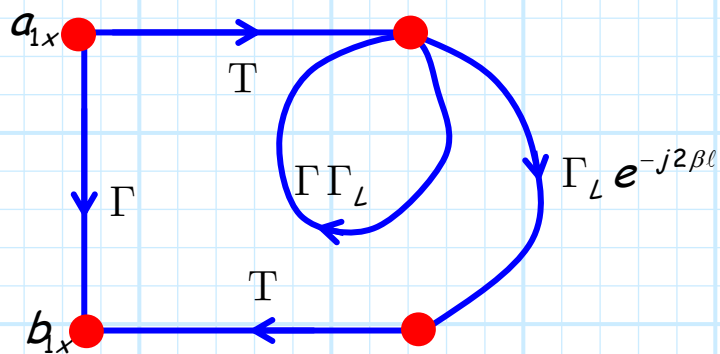


From the **self-loop** rule:

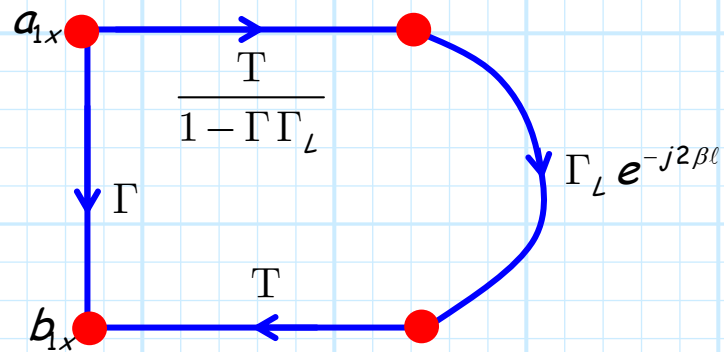

Again with the **series** rule:

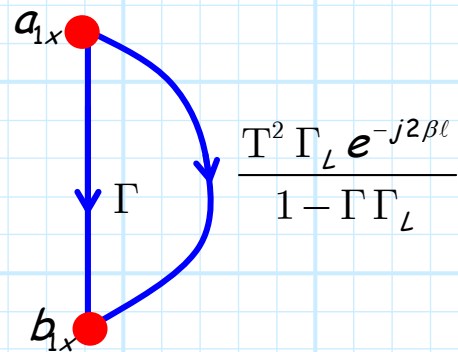

And finally with the **parallel** rule:

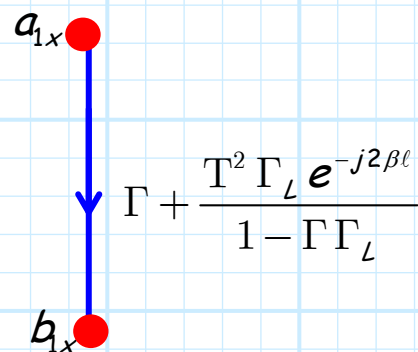

So that:

$$\Gamma_{in} \doteq \frac{b_{1x}}{a_{1x}} = \Gamma + \frac{T^2 \Gamma_L e^{-j2\beta\ell}}{1 - \Gamma\Gamma_L}$$

**Q:** Hey wait! If the quarter-wave transformer is a **matching network**, shouldn't  $\Gamma_{in} = 0$ ??

**A:** Who says it isn't! Consider now **three important facts**.

For a **quarter wave transformer**, we set  $Z_1$  such that:

$$Z_1^2 = Z_0 R_L \quad \Rightarrow \quad Z_0 = Z_1^2 / R_L$$

**Inserting** this into the scattering parameter  $S_{11}$  of the connector, we find:

$$\Gamma = \frac{Z_1 - Z_0}{Z_1 + Z_0} = \frac{Z_1 - Z_1^2/R_L}{Z_1 + Z_1^2/R_L} = \frac{R_L - Z_1}{R_L + Z_1}$$

Look at this result! For the quarter-wave transformer, the **connector  $S_{11}$  value** (i.e.,  $\Gamma$ ) is the **same** as the **load reflection coefficient  $\Gamma_L$** :

$$\Gamma = \frac{R_L - Z_1}{R_L + Z_1} = \Gamma_L \quad \leftarrow \text{Fact 1}$$

Since the connector is **lossless** (unitary scattering matrix!), we can conclude (and likewise show) that:

$$1 = |S_{11}|^2 + |S_{21}|^2 = |\Gamma|^2 + |T|^2$$

Since  $Z_0$ ,  $Z_1$ , and  $R_L$  are all real, the values  $\Gamma$  and  $T$  are also **real valued**. As a result,  $|\Gamma|^2 = \Gamma^2$  and  $|T|^2 = T^2$ , and we can likewise conclude:

$$\Gamma^2 + T^2 = 1 \quad \leftarrow \text{Fact 2}$$

Likewise, the Z1 transmission line has  $\ell = \lambda/4$ , so that:

$$2\beta\ell = 2\left(\frac{2\pi}{\lambda}\right)\frac{\lambda}{4} = \pi$$

where you of course recall that  $\beta = 2\pi/\lambda$ ! Thus:

$$e^{-j2\beta\ell} = e^{-j\pi} = -1 \quad \leftarrow \text{Fact 3}$$

As a result:

$$\Gamma_{in} = \Gamma + \frac{T^2 \Gamma_L e^{-j2\beta\ell}}{1 - \Gamma\Gamma_L} = \Gamma - \frac{T^2 \Gamma_L}{1 - \Gamma\Gamma_L}$$

And using the **newly discovered** fact that (for a correctly designed transformer)  $\Gamma_L = \Gamma$ :

$$\Gamma_{in} = \Gamma - \frac{T^2 \Gamma_L}{1 - \Gamma\Gamma_L} = \Gamma - \frac{T^2 \Gamma}{1 - \Gamma^2}$$

And also are **recent discovery** that  $T^2 = 1 - \Gamma^2$ :


$$\Gamma_{in} = \Gamma - \frac{T^2 \Gamma}{1 - \Gamma^2} = \Gamma - \frac{T^2 \Gamma}{T^2} = 0$$

**A perfect match!** The quarter-wave transformer does indeed work!


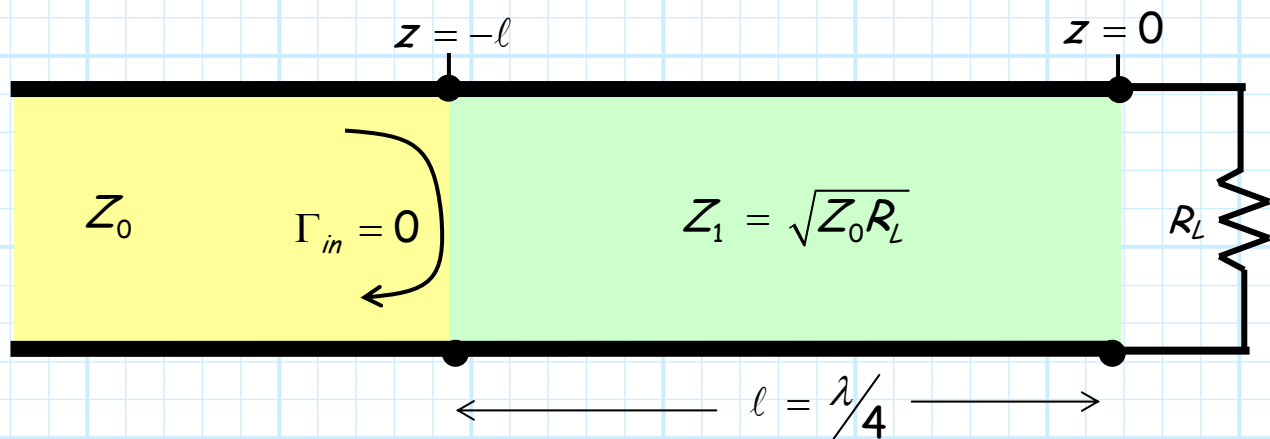
# Multiple Reflection Viewpoint


The **quarter-wave** transformer brings up an interesting question in  $\mu$ -wave engineering.




**Q:** *Why is there **no** reflection at  $z = -l$  ? It appears that the line is **mismatched** at both  $z = 0$  and  $z = -l$ .*

**A:** In fact there **are** reflections at these mismatched interfaces—an **infinite** number of them!

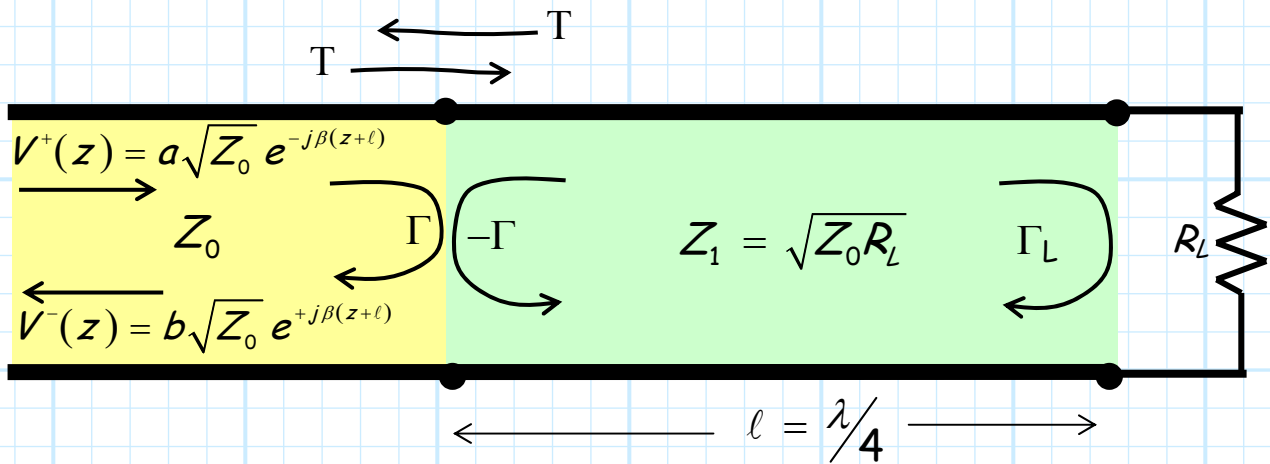
We can use our **signal flow graph** to determine the propagation series, once we determine all the **propagation paths** through the quarter-wave transformer.



$$b = a \sum_{n=1}^{\infty} p_n$$

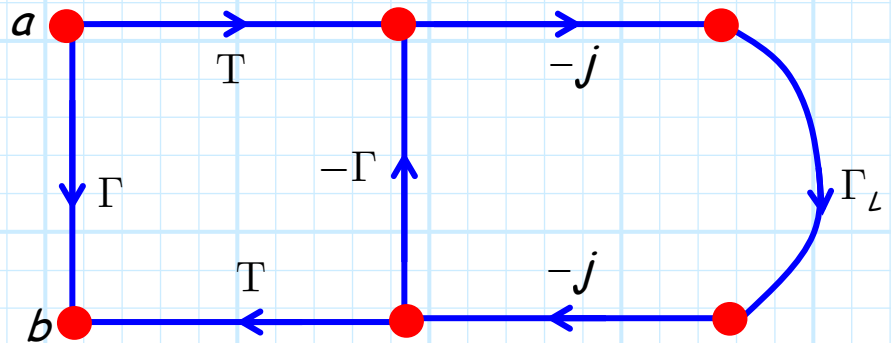


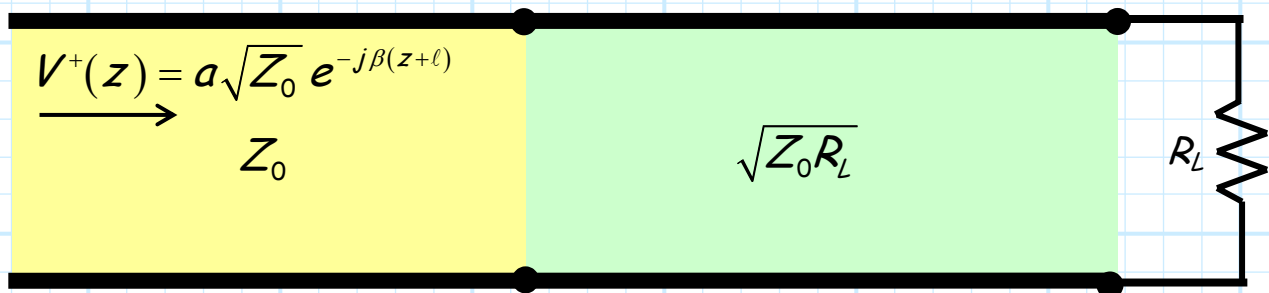Now let's try to interpret what **physically** happens when the **incident** voltage wave:




reaches the interface at  $z = -\ell$ . We find that there are **two forward paths** through the quarter-wave transformer signal flow graph.

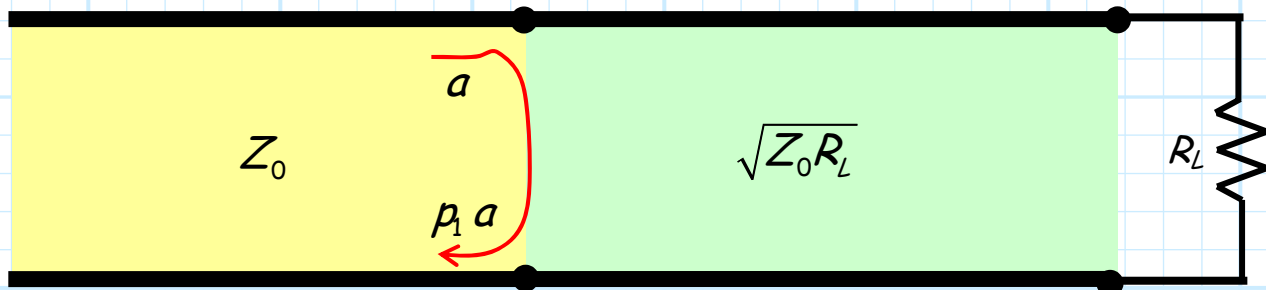
**Path 1.** At  $z = -l$ , the characteristic impedance of the transmission line changes from  $Z_0$  to  $Z_1$ . This mismatch creates a **reflected** wave, with complex amplitude  $\rho_1 a$ :



So,  $\rho_1 = \Gamma$ .

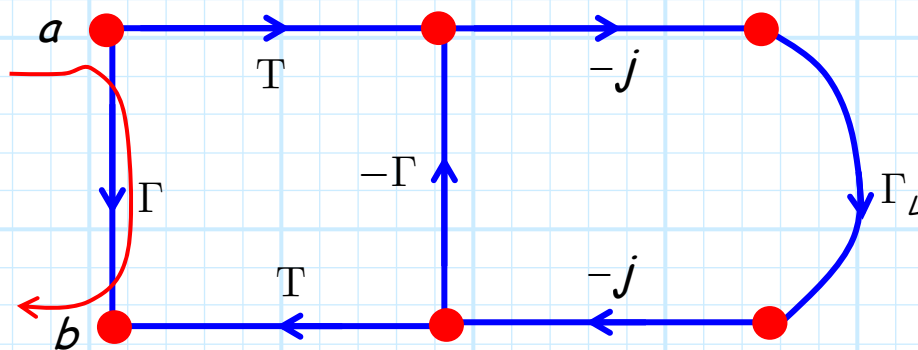


**Path 2.** However, a **portion** of the incident wave is transmitted (T) across the interface at  $z = -l$ , this wave travels a distance of  $\beta l = 90^\circ$  to the load at  $z = 0$ , where a portion of it is reflected ( $\Gamma_L$ ). This wave travels back  $\beta l = 90^\circ$  to the interface at  $z = -l$ , where a portion is again transmitted (T) across into the  $Z_0$  transmission line—**another** reflected wave!

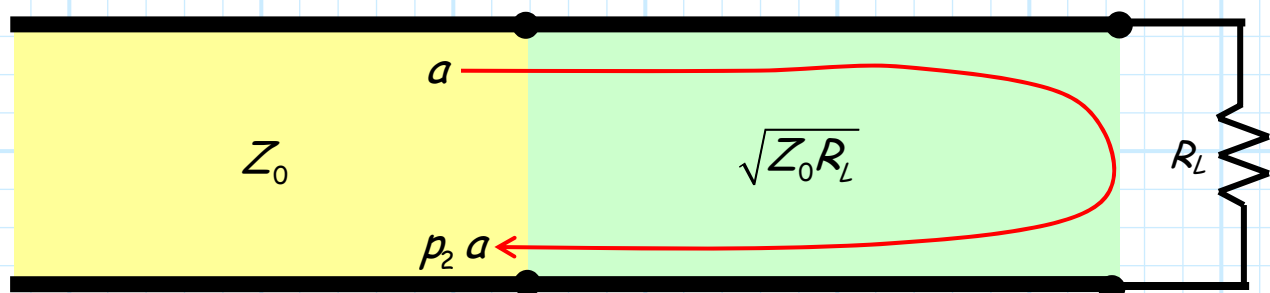


So the **second direct path** is

$$p_2 = T e^{-j90^\circ} \Gamma_L e^{-j90^\circ} T = -T^2 \Gamma_L$$

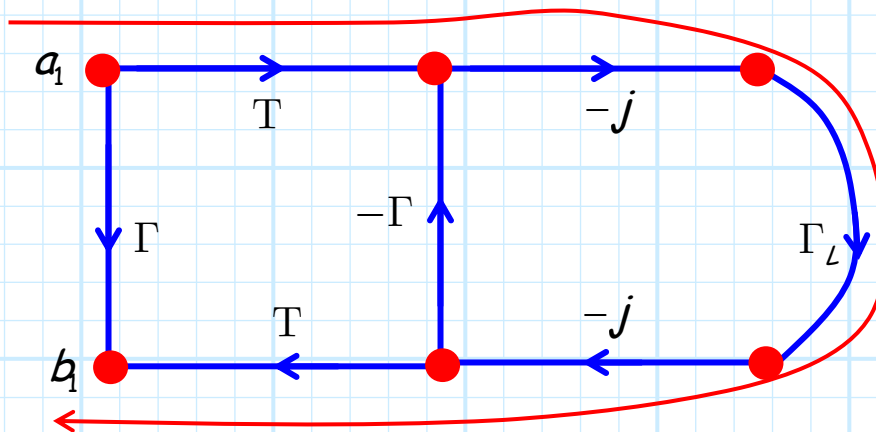note that traveling  $2\beta l = 180^\circ$  has produced a **minus** sign in the result.




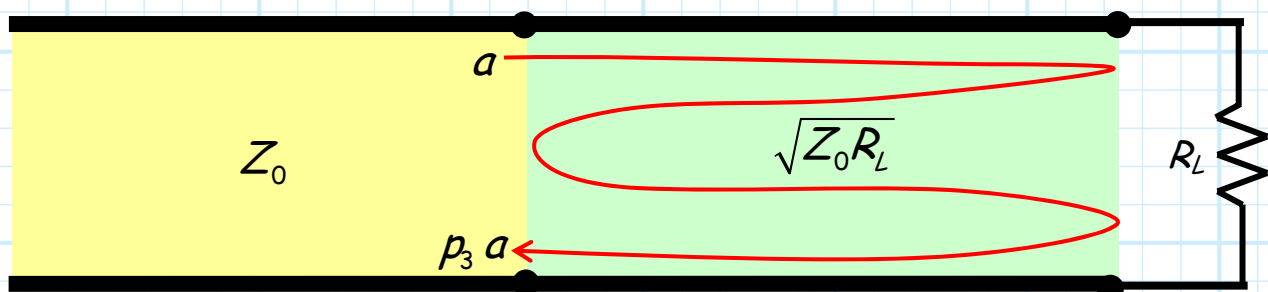**Path 3.** However, a **portion** of this **second** wave is also **reflected** ( $\Gamma$ ) back into the  $Z_1$  transmission line at  $z = -l$ , where it again travels to  $\beta l = 90^\circ$  the load, is partially reflected ( $\Gamma_L$ ), travels  $\beta l = 90^\circ$  back to  $z = -l$ , and is partially transmitted into  $Z_0$  ( $T$ )—our **third** reflected wave!



where:
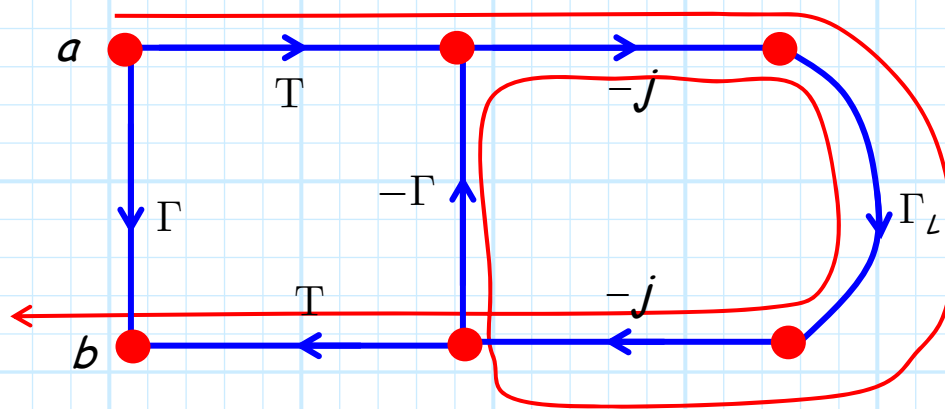
$$\begin{aligned} p_3 &= T e^{-j90^\circ} \Gamma_L e^{-j90^\circ} (-\Gamma) e^{-j90^\circ} \Gamma_L e^{-j90^\circ} T \\ &= -T^2 (\Gamma_L)^2 \Gamma \end{aligned}$$



Note that path 3 is **not** a direct path!

**Path  $n$ .** We can see that this "bouncing" back and forth can go on **forever**, with each trip launching a **new** reflected wave into the  $Z_0$  transmission line.

Note however, that the **power** associated with each successive reflected wave is **smaller** than the previous, and so eventually, the power associated with the reflected waves will **diminish** to insignificance!

**Q:** *But, why then is  $\Gamma = 0$  ?*

**A:** Each reflected wave is a **coherent** wave. That is, they all oscillate at same frequency  $\omega$ ; the reflected waves differ only in terms of their **magnitude** and **phase**.

Therefore, to determine the **total** reflected wave, we must perform a **coherent summation** of each reflected wave—this summation of course results in our **propagation series**, a series that must converge for passive devices.

$$b = a \sum_{n=1}^{\infty} p_n$$

It can be shown that the infinite propagation series for **this** quarter-wavelength structure **converges** to the closed-form expression:

$$\frac{b}{a} = \sum_{n=1}^{\infty} p_n = \frac{\Gamma - \Gamma^2 \Gamma_L - \Gamma^4 \Gamma_L}{1 - \Gamma^2}$$

Thus, the **input** reflection coefficient is:

$$\Gamma_{in} = \frac{b}{a} = \frac{\Gamma - \Gamma^2 \Gamma_L - \Gamma^4 \Gamma_L}{1 - \Gamma^2}$$

Using our definitions, it can likewise be shown that the **numerator** of the above expression is:

$$\Gamma - \Gamma^2 \Gamma_L - \Gamma^4 \Gamma_L = \frac{2(Z_1^2 - Z_0 R_L)}{(Z_1 + Z_0)(R_L + Z_1)}$$

It is evident that the numerator (and therefore  $\Gamma$ ) will be **zero** if:

$$Z_1^2 - Z_0 R_L = 0 \quad \Rightarrow \quad Z_1 = \sqrt{Z_0 R_L}$$

**Just** as we expected!

Physically, this results insures that all the reflected waves add coherently together to produce a **zero value!**

Note **all** of our transmission line analysis has been **steady-state** analysis. We assume our signals are **sinusoidal**, of the form  $\exp(j\omega t)$ . Note this signal exists for **all time**  $t$ —the signal is

assumed to have been "on" **forever**, and assumed to continue on forever.

In other words, in steady-state analysis, **all** the multiple reflections have long since occurred, and thus have reached a steady state—the reflected wave is **zero!**