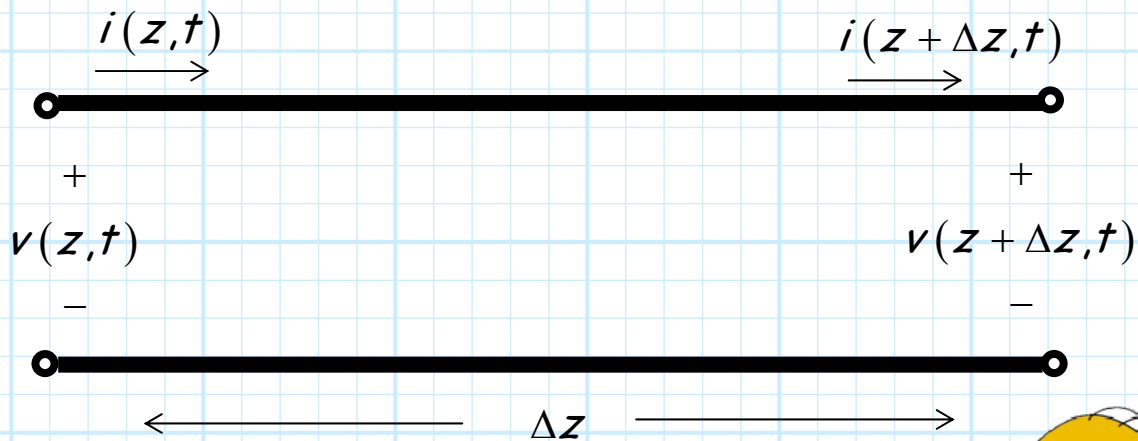


# The Telegrapher Equations


Consider a section of "wire":



Where:

$$i(z, t) \neq i(z + \Delta z, t)$$

$$v(z, t) \neq v(z + \Delta z, t)$$

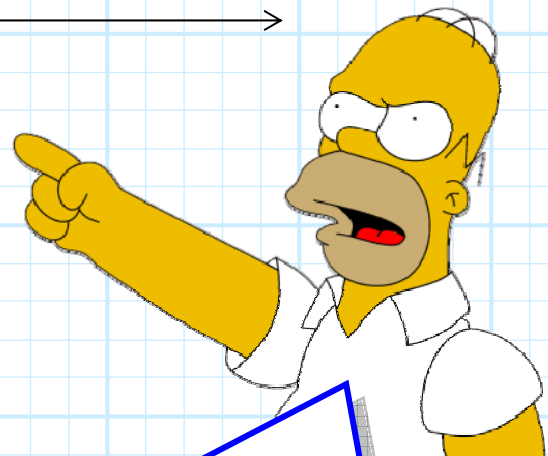


**Q:** No way! Kirchoff's Laws tells me that:

$$i(z, t) = i(z + \Delta z, t)$$

$$v(z, t) = v(z + \Delta z, t)$$

How can the voltage/current at the **end** of the line (at  $z + \Delta z$ ) be **different** than the voltage/current at the **beginning** of the line (at  $z$ )??

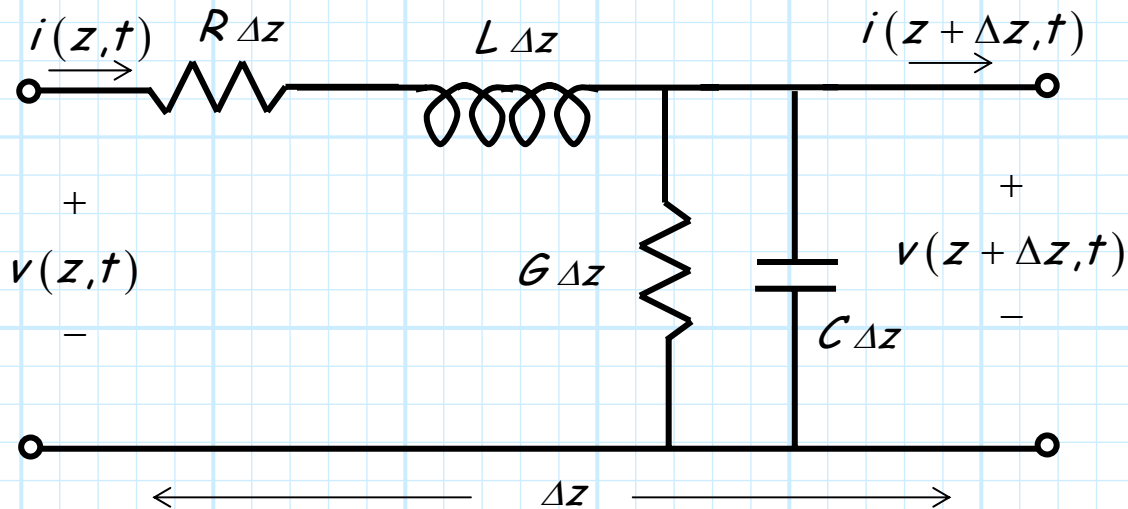**A:** Way. The structure above actually exhibits some non-zero value of **inductance, capacitance, conductance, and admittance!**  
A more accurate transmission line model is therefore:



Where:

$R$  = resistance/unit length

$L$  = inductance/unit length

$C$  = capacitance/unit length

$G$  = conductance/unit length

$\therefore$  resistance of wire length  $\Delta z$  is  $R\Delta z$

Now evaluating **KVL**, we find:

$$v(z + \Delta z, t) - v(z, t) = -R\Delta z i(z, t) - L\Delta z \frac{\partial i(z, t)}{\partial t} \neq 0$$

and from **KCL**:

$$i(z + \Delta z, t) - i(z, t) = -G\Delta z v(z, t) - C\Delta z \frac{\partial v(z, t)}{\partial t} \neq 0$$

Dividing the first equation by  $\Delta z$ , and then taking the limit as  $\Delta z \rightarrow 0$ :

$$\lim_{\Delta z \rightarrow 0} \frac{v(z + \Delta z, t) - v(z, t)}{\Delta z} = -R i(z, t) - L \frac{\partial i(z, t)}{\partial t}$$

which, by definition of the derivative, becomes:

$$\frac{\partial v(z, t)}{\partial z} = -R i(z, t) - L \frac{\partial i(z, t)}{\partial t}$$

Similarly, the KCL equation becomes:

$$\frac{\partial i(z, t)}{\partial z} = -G v(z, t) - C \frac{\partial v(z, t)}{\partial t}$$



These coupled differential equations are quite famous! Derived by **Oliver Heaviside**, they are known as the **telegrapher's equations**, and are essentially the Maxwell's equations of transmission lines.

$$\frac{\partial v(z, t)}{\partial z} = -R i(z, t) - L \frac{\partial i(z, t)}{\partial t}$$

$$\frac{\partial i(z, t)}{\partial z} = -G v(z, t) - C \frac{\partial v(z, t)}{\partial t}$$

Although **mathematically** the functions  $v(z, t)$  and current  $i(z, t)$  can take any form, they can **physically exist only if** they satisfy the both of the differential equations shown above!