

Special Problem 2.3-15

Determine the input impedance Z_{in} of the network below.

Make sure you **explain** how you arrived at this result!

Hint: Don't make this hard!

