

Special Problem 2.4-2

A lossless transmission line of length ℓ is terminated with a **normalized load impedance** of:

$$z'_L = 2.0 + jx_L.$$

All that is known about **load reactance** x_L is that it is **positive** ($x_L > 0$).

The **normalized input impedance** of this transmission line is:

$$z'_{in} = 0.2$$

Use a **Smith Chart** to determine the **length** of this transmission line in wavelengths.