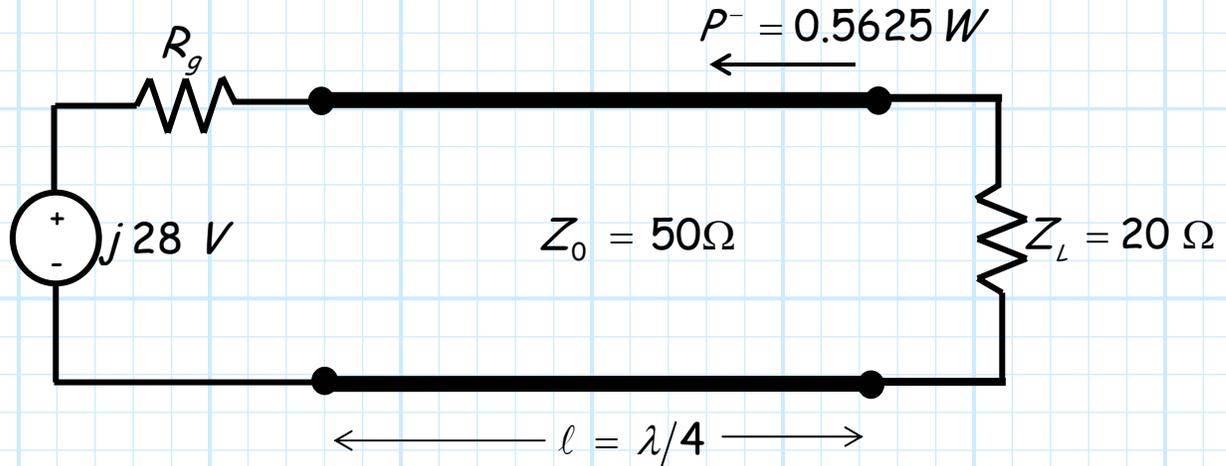


Special Problem 2.6-10

Consider this circuit, where the transmission line is **lossless** and has length $l = \lambda/4$:



The **generator impedance** is purely real (i.e., $Z_g = R_g + j0$)

The wave **reflected** from the load Z_L has power of $P^- = 0.5625 \text{ W}$.

Determine the generator resistance R_g .

Hint: This is **not** a boundary condition problem. Do **not** attempt to find $V(z)$ and/or $I(z)$!