

Special Problem 2.6-12

Determine the voltage $V(z)$ along the transmission line in the circuit below.

Hint: $V(z = -\lambda/4) \neq j4.5 V$

