

Special Problem 4.3-1

Determine the S-parameter matrix of this two port network. Note $Z_0 \neq Z_1$.

