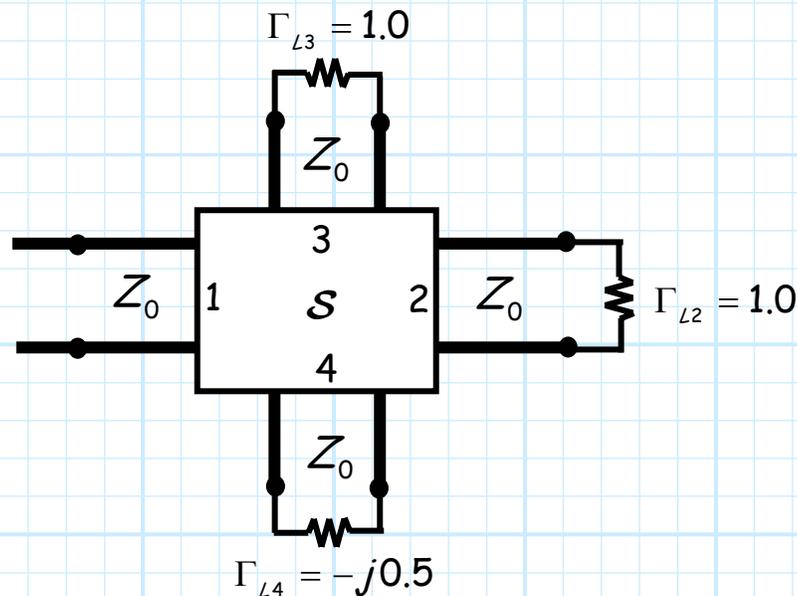


Special Problem 4.5-6

Three loads are connected to a non-reciprocal, **four-port** device.



The four-port device has the **scattering matrix**:

$$S = \begin{bmatrix} 0 & 0 & 0 & 0.7 \\ 0 & 0.5 & 0.8 & 0 \\ 0.25 & 0 & 0 & 0 \\ 0.2 & 0.5 & 0 & 0 \end{bmatrix}$$

1. Using the **nodes provide on the next page**, carefully and completely **draw** this signal flow graph of this network, including the **value** and **direction** of each and every (non-zero) **branch**.

2. Reduce this signal flow graph and determine the **total voltage** across the load at port 4 if $a_1 = 2.0$.

a_1



b_3



a_3



b_2



b_1



a_2



a_4



b_4

