

**Special Problem 5.5-4**

Consider the two-port network below.

Note the **lengths** of the transmission line sections!

Use the **theory of small reflections** to determine an **approximate, numeric value** of scattering parameter  $S_{22}$  (at the design frequency  $\omega_0 = v_p/\lambda_0$ ).

