

Design Project #2: Coupled Line Couplers

PROJECT SCOPE

Design a **coupled-line coupler** with the following specifications:

Number of sections	5
Center frequency	3 GHz
Coupling	12 dB
Port impedance	50 Ω
Frequency response	Maximally Flat

PROJECT TASKS:


1) Determine the **odd** and **even** mode impedances for each of the **5** sections. Implement this design in ADS.

2) Plot $|S_{11}|^2$, $|S_{21}|^2$, $|S_{31}|^2$ and $|S_{41}|^2$ (in **decibels**) from 0 to 6 GHz, using a vertical scale from -50 dB to 0 dB.

Q1: *Do these results indicate that your design is correct? Explain why you think so. Give **specific numerical examples** from each plot.*

3) Use the markers to determine the **bandwidth** of your design, given that the **coupling** must be numerically less than **15 dB** to satisfy specifications (i.e., a 3 dB bandwidth).

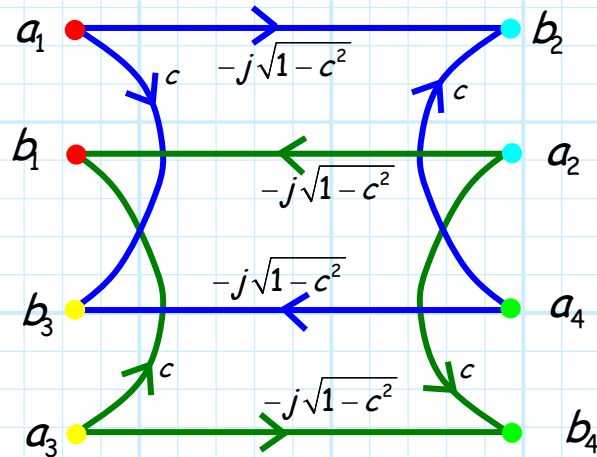4) Draw an **exact** signal flow graph of **this** (4-port) directional coupler. In other words, a signal flow graph of the form below, where c is the specific **coupling coefficient** of **this** coupler at the design frequency.



5) Reduce this signal flow graph for the case where ports 2, 3, and 4 are terminated in **matched loads** ($\Gamma_{L2} = \Gamma_{L3} = \Gamma_{L4} = 0$), and determine in **decibels** the numeric values of $|S_{11}|^2$, $|S_{21}|^2$, $|S_{31}|^2$ and $|S_{41}|^2$, at the **design frequency**.

Q2: Do these values **precisely match** those provided by the ADS analysis? **Why or why not?**

6) Now "attach" a **short circuit** ($\Gamma_{L4} = -1$) to **port 4** of the coupler **signal flow graph** (with ports 2 and 3 again terminated in matched loads). Reduce this graph and determine in **decibels** the numeric values of $|S_{11}|^2$, $|S_{21}|^2$, $|S_{31}|^2$, at the **design frequency**.

7) Likewise place a **short circuit** on port 4 of your ADS design—you now have a 3-port device! Replot $|S_{11}|^2$, $|S_{21}|^2$, $|S_{31}|^2$ (in dB) from 0 to 6 GHz, using the same vertical scale as before. Note you should **not** plot $|S_{41}|^2$!

Q3: *How do these new results compare to the case where port 4 is terminated in a matched load (i.e., tasks 2 and 5)? Use your knowledge of the physical behavior of coupled-line couplers—including any physical insight provided by the signal flow graph of task 6—to explain why you get this result. What physically happens to a wave incident on port 1, once it is inside the coupler?*

8) Now “attach” a short circuit ($\Gamma_{L4} = -1$) to port 2 of the coupler signal flow graph (with ports 2 and 4 terminated in matched loads). Reduce this graph and determine in decibels the numeric values of $|S_{11}|^2$, $|S_{31}|^2$, $|S_{41}|^2$, at the design frequency.

9) Likewise place a short circuit on port 2 of your ADS design—you now have a 3-port device! Replot $|S_{11}|^2$, $|S_{31}|^2$, $|S_{41}|^2$ (in dB) from 0 to 6 GHz, using the same vertical scale as before. Note you should **not** plot $|S_{21}|^2$!

Q4: *How do these new results compare to the case where port 2 is terminated in a matched load (i.e., tasks 2 and 5)? Use your knowledge of the physical behavior of coupled-line couplers—including any physical insight provided by the signal flow graph of task 8—to explain why you get this result. What physically happens to a wave incident on port 1, once it is inside the coupler?*

ADS INFORMATION

1. You will need to use four ADS “Term” elements (one for each coupler port).
2. You will need five “CLIN” elements, which are the ideal coupled transmission lines found in the “TLines-Ideal” element category.

3. The easiest way to attach a **short circuit** to a coupler port is to simply change the characteristic impedance of the "Term" element at that port (but only at that port!) to a value of $Z_0 = 0.1\Omega$ (0.1 ohm is as small as ADS will let you make Z_0). This of course is not exactly a short circuit, but it's pretty **close!**

Of course, you could likewise remove the "Term" element from a coupler port and then connect that port directly to a ground terminal. But, if you remove the "Term" element from a port, then ADS will renumber the remaining ports. For example, if you remove the "Term" element from port 2 and replace it with a short to ground (e.g., task 9), then the terminal at port three will be renamed port 2, and the terminal at port 4 will be renamed as port 3.

This in itself is not particularly bad, but you must make sure you are comparing "apples to apples" when comparing the results of task 2 to the results of task 9. For example, the values of task 9 that are labeled $|S_{21}|$ are actually $|S_{31}|$, if the "Term" element at port 2 is removed.

PROJECT REPORT

The same as project 1.

PROJECT GRADING

The same as project 1.