

# 11.2 Stability

**Reading Assignment: pp. 542-548**


A gain element is an active device. One potential problem with every active circuit is its stability

**HO: STABILITY**
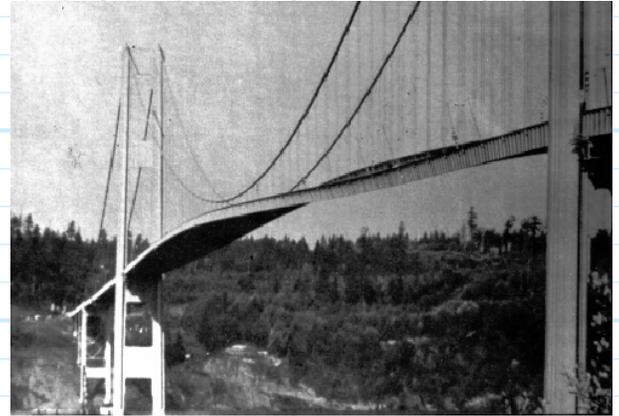
# Stability

**Q:** *So all there is to making a good microwave amplifier is the design of proper **matching networks**?*

**A:** There is one other problem that confronts the microwave amplifier designer. That problem is **stability** (of the amplifier, not the designer).



An unstable amplifier is also known as an **oscillator**—a source of microwave energy!

**Q:** *Under what **conditions** will an amplifier oscillate?*

**A:** An amplifier will go **unstable** if **either** of these two conditions are true:

$$|\Gamma_{out}| = \left| S_{22} + \frac{S_{12}S_{21}\Gamma_s}{1 - S_{11}\Gamma_s} \right| > 1.0$$

$$|\Gamma_{in}| = \left| S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} \right| > 1.0$$

In other words, the amplifier will oscillate if either the input or output reflection coefficient of the gain element has a **magnitude greater than one**.

**Q:** *Hey wait! I thought we learned that the **maximum** value of any reflection coefficient magnitude was 1 (i.e.,  $|\Gamma| \leq 1.0$ )—this defined the **validity region** of our Smith Chart!*

**A:** Remember, the inequality  $|\Gamma| \leq 1.0$  is true for any **passive** load or device. Our gain element is an **active** device—it must have a DC source of power.

As a result, we find that  $|\Gamma| > 1.0$  is quite **possible**!

**Q:** *But, we learned that the region outside the  $|\Gamma| = 1.0$  circle on the Smith Chart corresponded to loads with **negative values of resistance**. Does this mean that  $Z_{in}$  or  $Z_{out}$  could have real (i.e. resistive) components that are **negative**?*

**A:** That's **exactly** what it means!

**Q:** *What is a negative resistor exactly?*

**A:** Ohm's law **still** applies—negative resistance or not. As a result, we would find for a  $-10 \Omega$  resistor that:

$$\frac{V}{I} = -10 \quad \Rightarrow \quad V = -10I$$

**Q:** ???

**A:** The result above simply means that the current through a negative resistor is  $180^\circ$  **out-of-phase** with the voltage across it.

→ The resistor current is at its minimum value when the voltage across it is at its maximum—and **vice versa!**

This behavior drives our amplifier circuit a little **wacky**, and it begins to oscillate!

**Q:** *So how do we **avoid** this unfortunate occurrence?*

**A:** Recall that amplifier instability occurs when:

$$|\Gamma_{out}| = \left| S_{22} + \frac{S_{12}S_{21}\Gamma_s}{1 - S_{11}\Gamma_s} \right| > 1.0$$

$$|\Gamma_{in}| = \left| S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} \right| > 1.0$$


Thus, for a **given** gain element (i.e.,  $S_{11}, S_{21}, S_{22}, S_{12}$ ), amplifier stability is determined by the value of  $\Gamma_L$  and  $\Gamma_s$ .

We can **solve** the above equations to determine the specific range of values of  $\Gamma_L$  and  $\Gamma_s$  that will **induce oscillation**. The results are provided in page 543 and 544 of your text.

We find that these unstable values—when plotted on the **complex  $\Gamma$  plane**—form a circle. These circles are known as **stability circles**.



These gain circles are defined as a complex value  $C$ , which specifies the location of the stability circle **center** on the complex  $\Gamma$  plane, and a real value  $R$ , which specifies the **radius** of the stability circle.

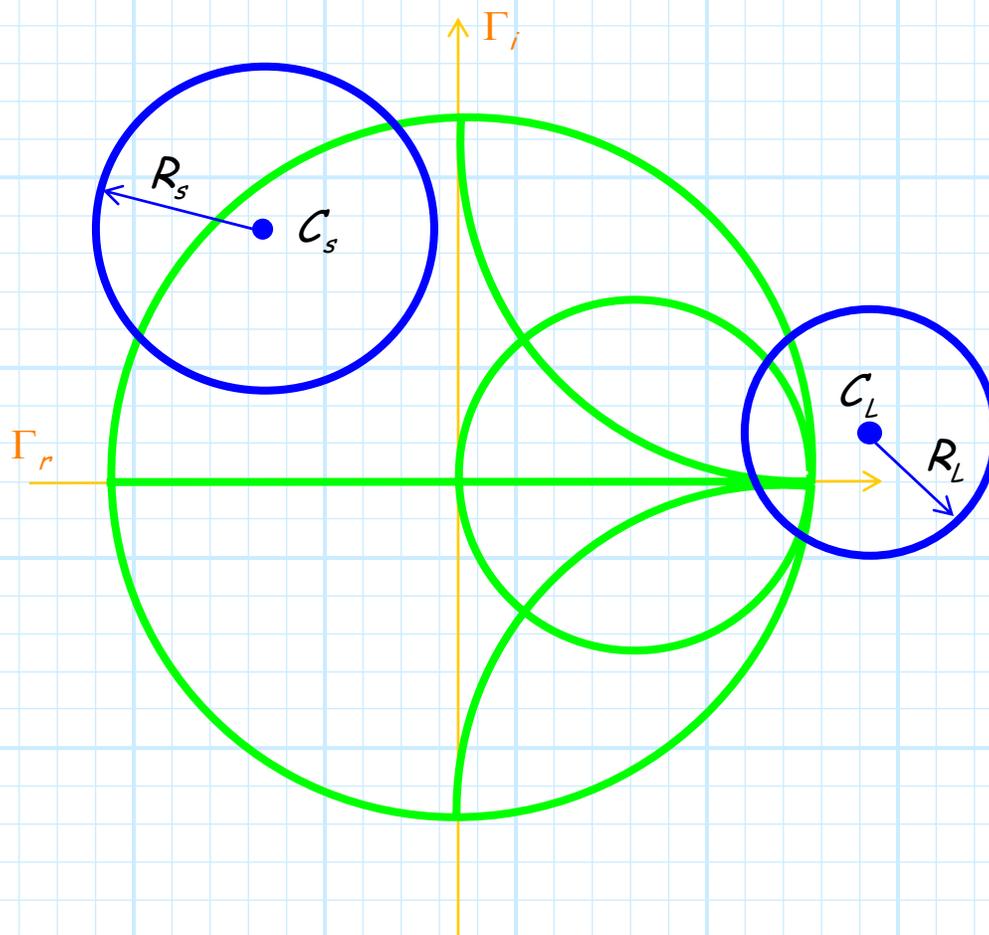There is **one** stability circle for  $\Gamma_L$  (i.e.,  $C_L$  and  $R_L$ ) and **another** for  $\Gamma_S$  (i.e.,  $C_S$  and  $R_S$ ). Typically, the  $\Gamma$  values that lie **inside** the circle will create amplifier oscillation.



**Q:** *So what do we use these stability circles for?*

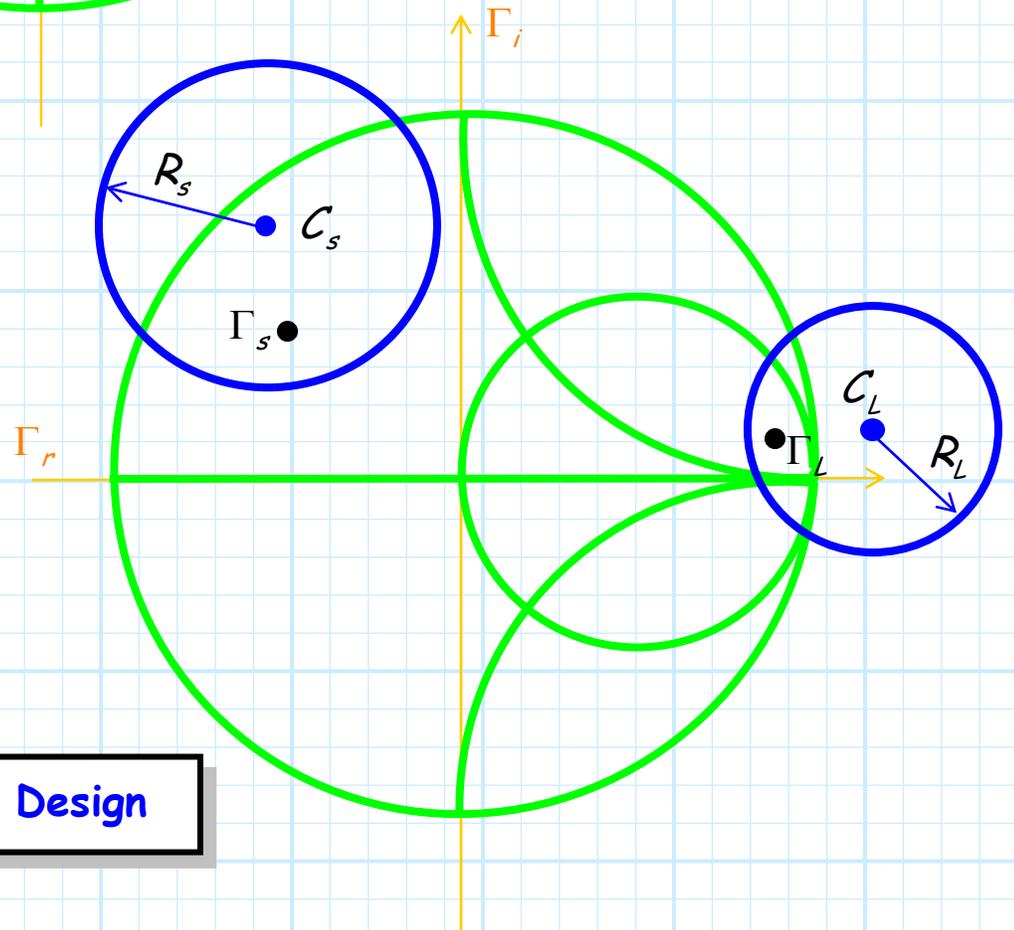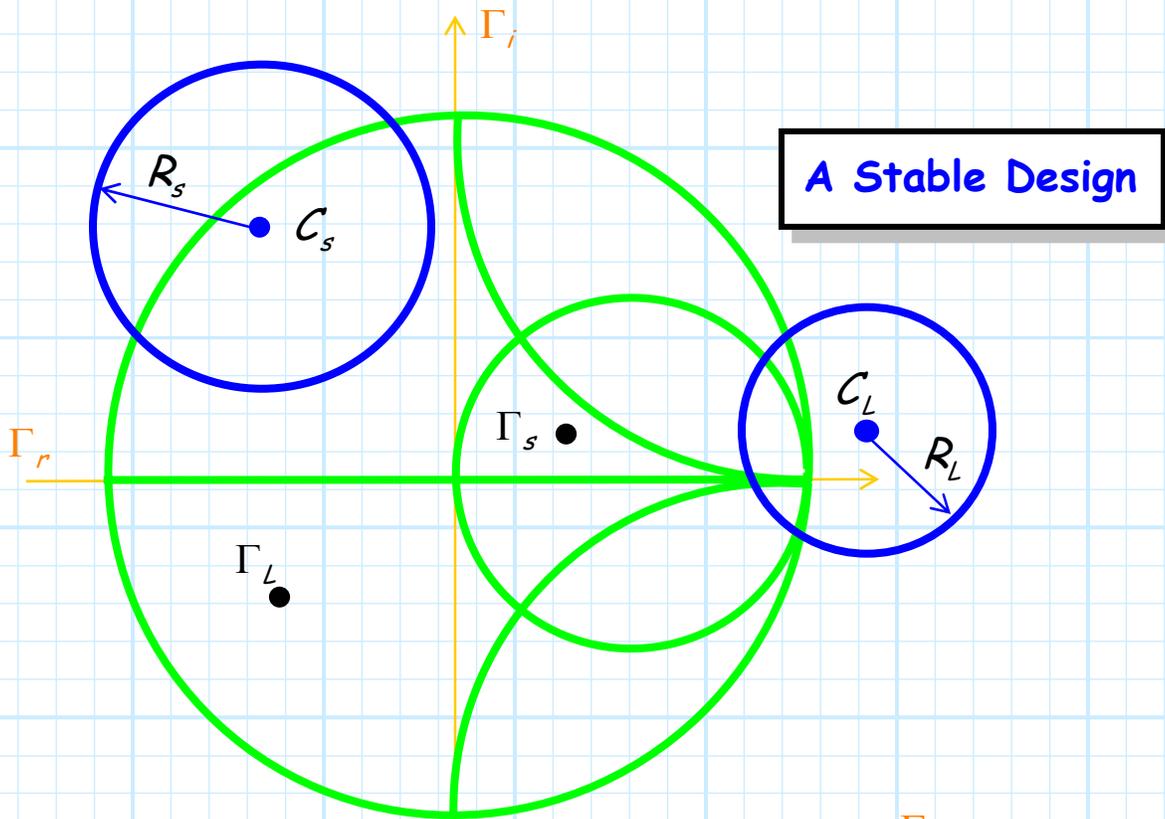**A:** As an amplifier designer, we must make sure that our **design values**  $\Gamma_L$  and  $\Gamma_S$  lie **outside** these circles—otherwise, our well-designed amplifiers will **oscillate!**




**Q:** *Yikes! Must we **always** determine these circles and check our design for instability?*

**A:** Not necessarily! Some gain elements are **unconditionally stable**. As the name suggests, these gain elements result in stable amplifiers for any and all **realizable** values of  $\Gamma_L$  and  $\Gamma_S$ .

**Q:** *So an unconditionally stable gain element has stability circles with **zero radius** (i.e.,  $R = 0$ )?*

**A:** **Could** be, but all that is required for a gain element to be unconditionally stable is for its stability circles to lie completely **outside** the  $|\Gamma| = 1$  circle.

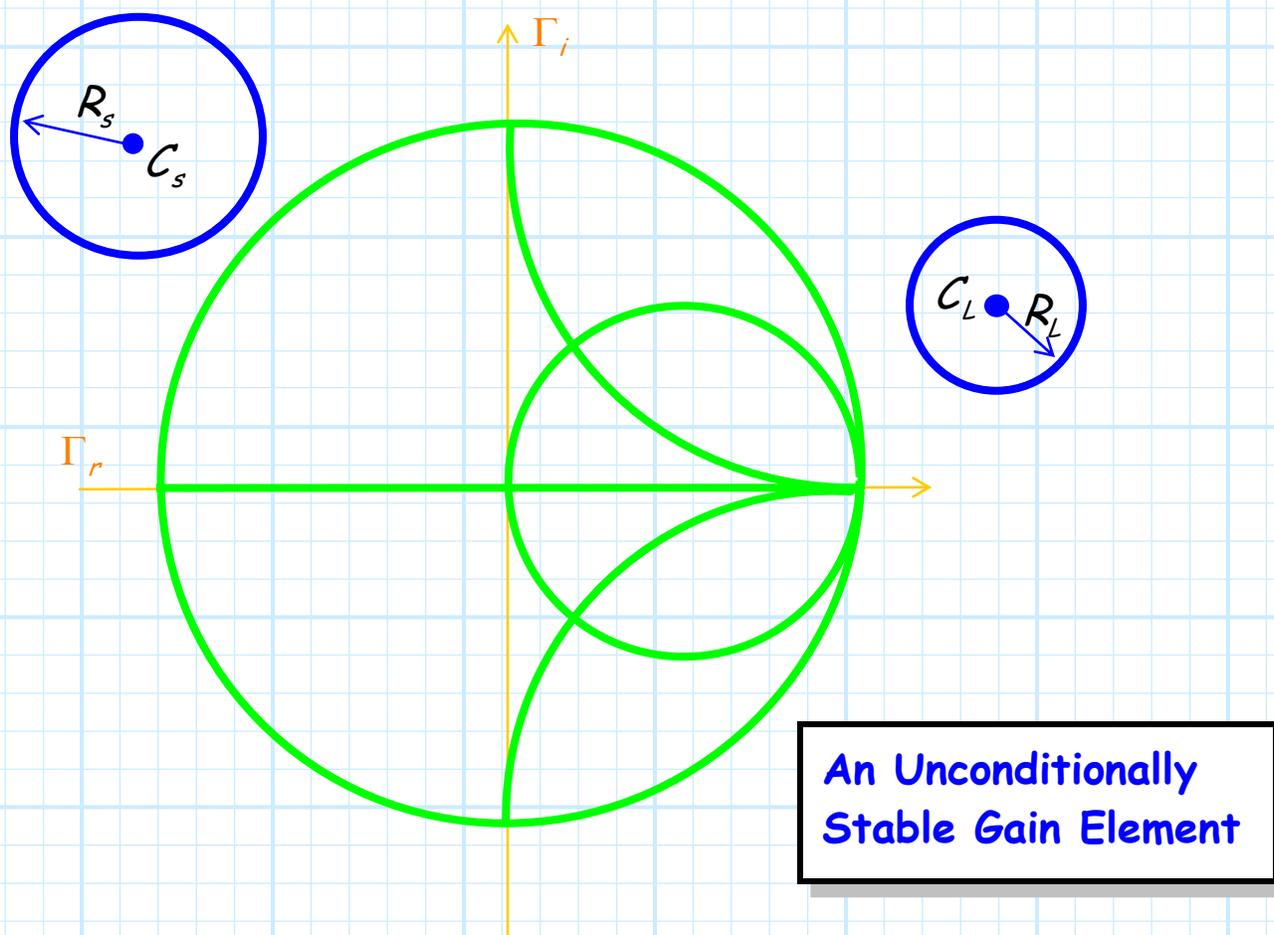

For this condition, we find that the values of  $\Gamma_L$  and  $\Gamma_s$  that result in an unstable amplifier must have a magnitude **greater than 1** (i.e.,  $|\Gamma_L| > 1$  or  $|\Gamma_s| > 1$ ).

But, we can presume that our the loads and sources attached to our amplifier will **always** have **positive** resistances, such that  $|\Gamma_L| < 1$  and  $|\Gamma_s| < 1$ .

Thus, an **amplifier** constructed with an unconditionally stable gain element will likewise be **unconditionally stable!**

**Q:** *How will I recognize an unconditionally stable gain element if I see one? Must I determine and plot the stability circles?*

**A:** There are **tests** that we can apply—using the scattering parameters  $S_{11}, S_{21}, S_{22}, S_{12}$ —to more **directly** determine if a gain element is unconditionally stable.

First, we find some **necessary conditions** for a gain element to be unconditionally stable are:


$$|S_{11}|^2 < 1 \quad \text{and} \quad |S_{22}|^2 < 1$$

If our gain element is **unilateral** (i.e.,  $S_{12} = 0$  or approx.  $|S_{12}| \ll |S_{21}|$ ) then the above conditions are likewise **sufficient** for unconditional stability.


Otherwise, (for  $S_{12} \neq 0$ ) we find that our gain element must pass **two more tests**—tests that are provided on page 545 of your text.

**Q:** Do we really *care* if our design is unconditionally stable? Aren't we really *just* concerned with whether our design values  $\Gamma_L$  and  $\Gamma_s$  lie inside the stability circle?

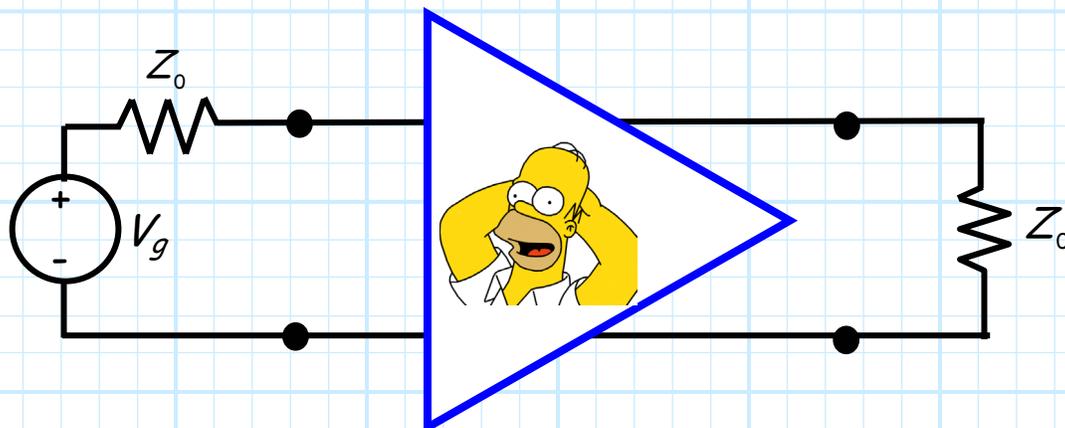**A:** Remember, the values  $\Gamma_L$  and  $\Gamma_s$  are determined for the **specific** values of source and load impedances connected to the amplifier (**presumably**  $Z_0$ ).



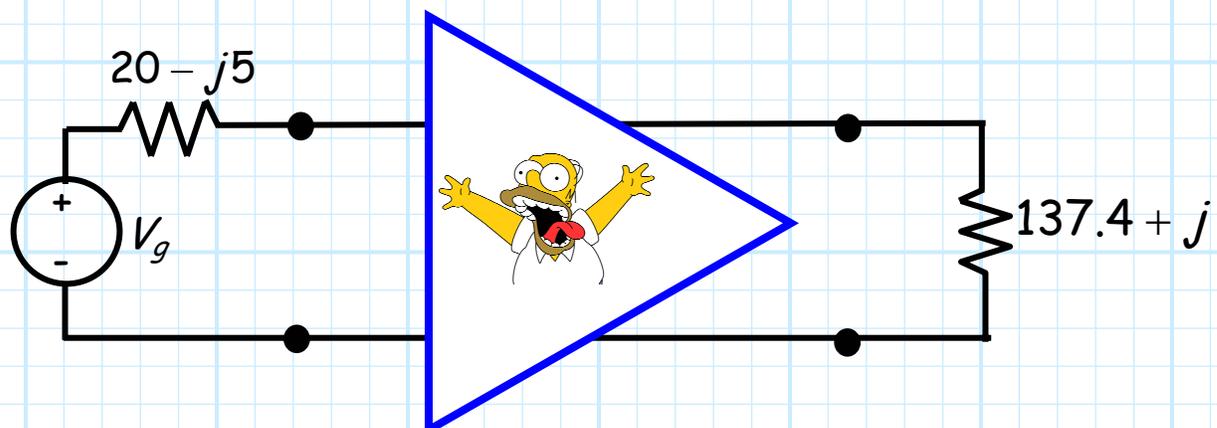But what if the resulting amplifier is **not** connected to these ideal sources? The ideal source or load impedance  $Z_0$  is **never** achieved with **perfection**, and often achieved **not at all** (consider all the **narrow-band** devices we have studied!).



Thus, since we **do not specifically** know what source and load impedances our amplifier might encounter, we had generally design an amplifier that is stable for them **all**—one that's **unconditionally stable!**

**Q:** *Anything else we need to know about amplifier stability?*

**A:** One last **very** important thing.

Recall that amplifiers, like all microwave devices, are **dependent on frequency**. Thus, all of the important values involved in our design (e.g.,  $\Gamma_s$ ,  $S_{11}$ ,  $S_{21}$ ,  $S_{22}$ ,  $S_{12}$ ,  $\Gamma_o$ ) will **change** as a function of frequency!

**Q:** *I see, amplifier performance, most notably **gain**, will change as a function of frequency, and so maximum power transfer will occur at just our **design frequency**.*

*We've seen this kind of thing **before!***

**A:** **True**, but for amplifiers there is also a **new** twist.

The amplifier stability conditions (i.e., stability tests) must be satisfied at **any and all frequencies!**

If for **even one frequency** we find that either:

$$|\Gamma_{out}| = \left| S_{22} + \frac{S_{12} S_{21} \Gamma_s}{1 - S_{11} \Gamma_s} \right| > 1.0 \quad \text{or} \quad |\Gamma_{in}| = \left| S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L} \right| > 1.0$$

then our amplifier will **oscillate—even** if that frequency is **not** our "design frequency"!

This makes amplifier stability a much more **significant** and **difficult** problem than you might otherwise think.

→ An unconditionally stable amplifier must be unconditionally stable at **all frequencies!**