Special Problem 10.3-1

Find the Boolean logic function which describes this **pull-down network (PDN)** from a CMOS logic device.